

# CIS 5710


## Computer Organization and Design

### Unit 3: Arithmetic

Based on slides by Profs. Amir Roth & Milo Martin & C.J. Taylor

# This Unit: Arithmetic

---

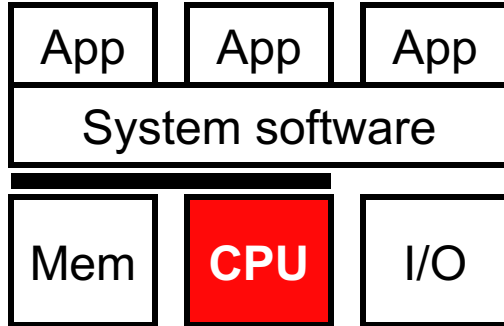


- A little review
  - Binary + 2s complement
  - Ripple-carry addition (RCA)
- Fast integer addition
  - Carry-select (CSeA)
  - Carry Lookahead Adder (CLA)
- Shifters
- Integer multiplication and division
- Floating point arithmetic

# Readings

---

- P&H
  - Chapter 3

# The Importance of Fast Arithmetic

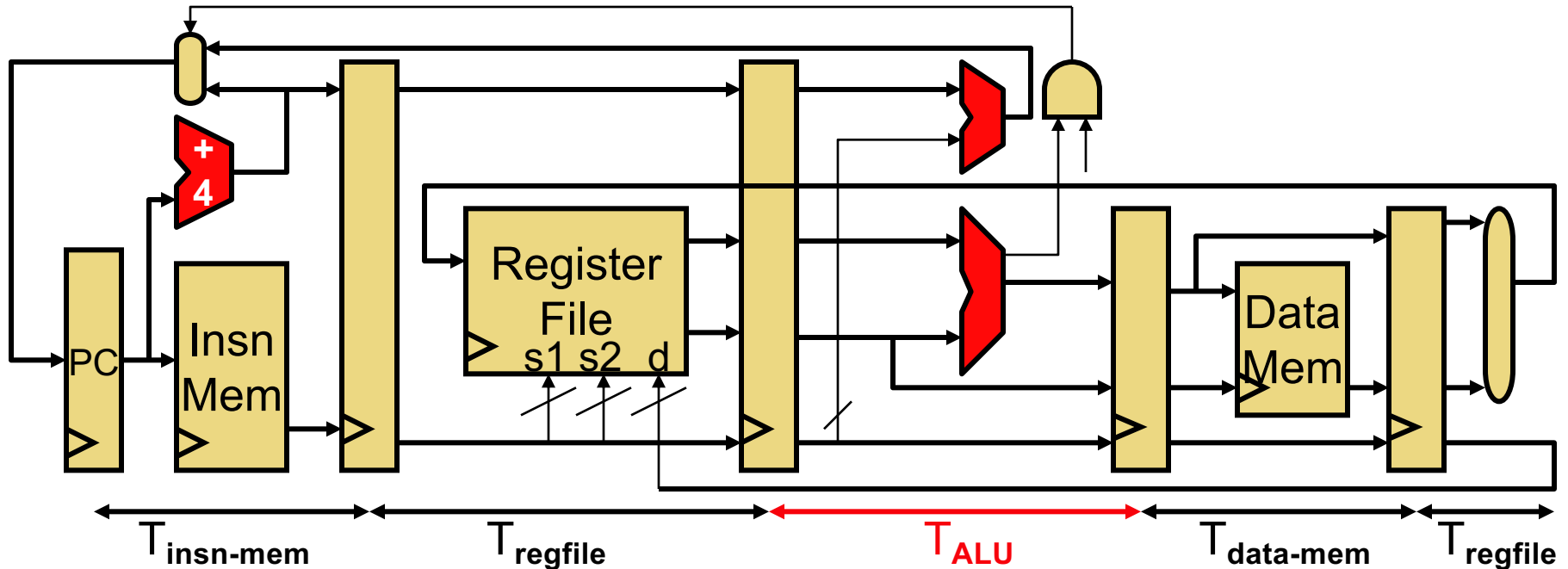

- Addition of two numbers is most common operation
  - Programs use addition frequently
  - Loads and stores use addition for address calculation
  - Branches use addition to test conditions and calculate targets
  - All insns use addition to calculate default next PC
- Fast addition is critical to high performance

# Review: Binary Integers

---

- Computers represent integers in binary (base2)

$$3 = 11, 4 = 100, 5 = 101, 30 = 11110$$

+ Natural since only two values are represented

- Addition, etc. take place as usual (carry the 1, etc.)

$$17 = 10001$$

$$\begin{array}{r} +5 = 101 \\ \hline \end{array}$$

$$22 = 10110$$

- Some old machines use decimal (base10) with only 0/1

$$30 = 011\ 000$$

- Often called BCD (binary-coded decimal)
  - Unnatural for digital logic, implementation complicated & slow
  - + Required for precise currency operations

# Fixed Width

---

- On pencil and paper, integers have infinite width
- In hardware, integers have **fixed width**
  - N bits: 16, 32 or 64
  - LSB is  $2^0$ , MSB is  $2^{N-1}$
  - **Range**: 0 to  $2^N - 1$
  - Numbers  $> 2^N$  represented using multiple fixed-width integers
    - In software (e.g., Java BigInteger class)

# What About Negative Integers?

---

- **Sign/magnitude**

- Unsigned plus one bit for sign  
10 = 000001010, -10 = 100001010
- + Matches our intuition from “by hand” decimal arithmetic
- representations of both +0 and -0
- Addition is difficult
- symmetric range:  $-(2^{N-1}-1)$  to  $2^{N-1}-1$

- Option II: **two's complement (2C)**

- Leading 0s mean positive number, leading 1s negative  
10 = 00001010, -10 = 11110110
- + One representation for 0 (all zeroes)
- + Easy addition
- asymmetric range:  $-(2^{N-1})$  to  $2^{N-1}-1$

# The Tao of 2C

---

- How did 2C come about?
  - “Let’s design a representation that makes addition easy”
  - Think of subtracting 10 from 0 by hand with 8-bit numbers
  - Have to “borrow” 1s from some imaginary leading 1

$$\begin{array}{rcl} 0 & = & 100000000 \\ -10 & = & 00000010 \\ \hline -10 & = & 011111110 \end{array}$$

- Now, add the conventional way...

$$\begin{array}{rcl} -10 & = & 11111110 \\ +10 & = & 00000010 \\ \hline 0 & = & 100000000 \end{array}$$



# Still More On 2C

---

- What is the interpretation of 2C?
  - Same as binary, except **MSB represents  $-2^{N-1}$** , not  $2^{N-1}$ 
    - $-10 = 11110110 = -2^7 + 2^6 + 2^5 + 2^4 + 2^2 + 2^1$
  - + Extends to any width
    - $-10 = 110110 = -2^5 + 2^4 + 2^2 + 2^1$
    - Why?  $2^N = 2 * 2^{N-1}$
    - $-2^5 + 2^4 + 2^2 + 2^1 = (-2^6 + 2 * 2^5) - 2^5 + 2^4 + 2^2 + 2^1 = -2^6 + 2^5 + 2^4 + 2^2 + 2^1$
  - Equivalent to computing modulo  $2^N$
- Trick to negating a number quickly:  **$-B = B' + 1$** 
  - $-(1) = (0001)' + 1 = 1110 + 1 = 1111 = -1$
  - $-(-1) = (1111)' + 1 = 0000 + 1 = 0001 = 1$
  - $-(0) = (0000)' + 1 = 1111 + 1 = 0000 = 0$
  - Think about why this works

# Addition

# 1st Grade: Decimal Addition

---

$$\begin{array}{r} 1 \\ 43 \\ +29 \\ \hline 72 \end{array}$$

- Repeat N times
  - Add least significant digits and any overflow from previous add
  - Carry “overflow” to next decimal place
    - **Overflow**: any digit other than least significant of sum
  - Both two addends and the sum are shifted right by one
- Sum of two N-digit numbers can yield an N+1 digit number

# Binary Addition: Works the Same Way

---

$$\begin{array}{r} 1 \quad 111111 \\ 43 = 00101011 \\ +29 = 00011101 \\ \hline 72 = 01001000 \end{array}$$


- Repeat N times
    - Add least significant bits and any overflow from previous add
    - Carry the overflow to next addition
    - Shift two addends and sum one bit to the right
  - Sum of two N-bit numbers can yield an N+1 bit number
- More steps (smaller base)
- + Each one is simpler (adding just 1 and 0)

# The Half Adder

- How to add two binary integers in hardware?
- Start with adding two bits
  - When all else fails ... look at truth table

<u>A</u>	<u>B</u>	<u>=</u>	<u>C0</u>	<u>S</u>
0	0	=	0	0
0	1	=	0	1
1	0	=	0	1
1	1	=	1	0

 
- **$S = A \oplus B$**
- **CO (carry out) =  $AB$**
- This is called a **half adder**



# The Other Half

- We could chain half adders together, but to do that...
  - Need to incorporate a carry out from previous adder


<u>C</u>	<u>A</u>	<u>B</u>	=	<u>CO</u>	<u>S</u>
0	0	0	=	0	0
0	0	1	=	0	1
0	1	0	=	0	1
0	1	1	=	1	0
1	0	0	=	0	1
1	0	1	=	1	0
1	1	0	=	1	0
1	1	1	=	1	1

 

- $S = C'A'B \mid C'AB' \mid CA'B' \mid CAB = C \wedge A \wedge B$
- $CO = C'AB \mid CA'B \mid CAB' \mid CAB = CA \mid CB \mid AB$
- This is called a **full adder**
 
# Ripple-Carry Adder

- N-bit **ripple-carry** adder
  - N 1-bit full adders “chained” together
    - $CO_0 = CI_1, CO_1 = CI_2$ , etc.
    - $CI_0 = 0$
    - $CO_{N-1}$  is carry-out of entire adder
      - $CO_{N-1} = 1 \rightarrow$  “overflow”
- Example: 16-bit ripple carry adder
  - How fast is this?
  - How fast is an N-bit ripple-carry adder?



# Quantifying Adder Delay


---

- Combinational logic dominated by **gate delays**
  - How many gates between input and output?
  - Array storage dominated by wire delays
  - Longest delay or **critical path** is what matters
- Can implement any combinational function in “2” logic levels
  - 1 level of AND + 1 level of OR (PLA)
  - NOTs are “free”: push to input (DeMorgan’s) or read from latch
  - Example:  $\text{delay}(\text{FullAdder}) = 2$ 
    - $d(\text{CarryOut}) = \text{delay}(AB \mid AC \mid BC)$
    - $d(\text{Sum}) = d(A \wedge B \wedge C) = d(AB'C' \mid A'BC' \mid A'B'C \mid ABC) = 2$
    - Note ‘ $\wedge$ ’ means Xor (just like in C & Java)
- Caveat: “2” assumes gates have few (<8 ?) inputs


 
# Ripple-Carry Adder Delay

- Longest path is to  $CO_{15}$  (or  $S_{15}$ )
  - $\text{delay}(CO_{15}) = 2 + \text{MAX}(d(A_{15}), d(B_{15}), d(CI_{15}))$ 
    - $d(A_{15}) = d(B_{15}) = 0$ ,  $d(CI_{15}) = d(CO_{14})$
  - $d(CO_{15}) = 2 + d(CO_{14}) = 2 + 2 + d(CO_{13}) \dots$
  - **$d(CO_{15}) = 32$**
- **$d(CO_{N-1}) = 2N$** 
  - **Too slow!**
  - **Linear in number of bits**
- Number of gates is also linear



# Division

# 4th Grade: Decimal Division

---

$\begin{array}{r} \phantom{0}9 \\ 3 \overline{)29} \\ \underline{-27} \\ 2 \end{array}$	// quotient
	// divisor   dividend
	// remainder

- Shift divisor left (multiply by 10) until MSB lines up with dividend's
- Repeat until remaining dividend (remainder) < divisor
  - Find largest single digit  $q$  such that  $(q * \text{divisor}) < \text{dividend}$
  - Set LSB of quotient to  $q$
  - Subtract  $(q * \text{divisor})$  from dividend
  - Shift quotient left by one digit (multiply by 10)
  - Shift divisor right by one digit (divide by 10)

# Binary Division

---

$$\begin{array}{r} \underline{\phantom{00}3} \overline{)29} = 0011 \quad \underline{\phantom{00}1001} = \underline{\phantom{00}9} \\ \underline{-24} = \quad \underline{-011000} \\ \phantom{00}5 = \quad \phantom{00}000101 \\ \underline{-3} = \quad \underline{-000011} \\ \phantom{00}2 = \quad \phantom{00}000010 \end{array}$$

# Binary Division Hardware

---

- Same as decimal division, except (again)
  - More individual steps (base is smaller)
  - + Each step is simpler
  - Find largest bit  $q$  such that  $(q * \text{divisor}) < \text{dividend}$ 
    - $q = 0$  or  $1$
  - Subtract  $(q * \text{divisor})$  from dividend
    - $q = 0$  or  $1 \rightarrow$  no actual multiplication, subtract divisor or not
- Complication: **largest**  $q$  such that  $(q * \text{divisor}) < \text{dividend}$ 
  - How do you know if  $(1 * \text{divisor}) < \text{dividend}$ ?
  - Human can “eyeball” this
  - Computer does not have eyeballs
    - it must subtract and see if result is negative

# Software Divide Algorithm

---

- Can implement this algorithm in software
  - Inputs: dividend and divisor
  - Outputs: quotient = dividend / divisor  
rem = dividend % divisor
- ```
remainder = 0;
quotient = 0;
for (int i = 0; i < 32; i++) {
    remainder = (remainder << 1) | (dividend >> 31);
    if (remainder >= divisor) {
        quotient = (quotient << 1) | 1;
        remainder = remainder - divisor;
    } else {
        quotient = (quotient << 1) | 0;
    }
    dividend = dividend << 1;
}
```

# Divide Example


---

- Input: Divisor = 00011 , Dividend = 11101

| Step | Remainder                                           | Quotient                                | Remainder                              | Dividend                                            |
|------|-----------------------------------------------------|-----------------------------------------|----------------------------------------|-----------------------------------------------------|
| 0    | 00000                                               | 00000                                   | 00000                                  | <span style="border: 1px solid blue;">1</span> 1101 |
| 1    | 0000 <span style="border: 1px solid blue;">1</span> | 0000 <span style="color: red;">0</span> | 00001                                  | <span style="color: red;">1</span> 1010             |
| 2    | 0001 <span style="color: red;">1</span>             | 0000 <span style="color: red;">1</span> | <span style="color: red;">00000</span> | <span style="color: red;">1</span> 0100             |
| 3    | 0000 <span style="color: red;">1</span>             | 0001 <span style="color: red;">0</span> | 00001                                  | <span style="color: red;">0</span> 1000             |
| 4    | 0001 <span style="color: red;">0</span>             | 0010 <span style="color: red;">0</span> | 00010                                  | <span style="color: red;">1</span> 0000             |
| 5    | 0010 <span style="color: red;">1</span>             | 0100 <span style="color: red;">1</span> | <span style="color: red;">00010</span> | 00000                                               |

- Result: Quotient: 1001, Remainder: 10

# Divider Circuit

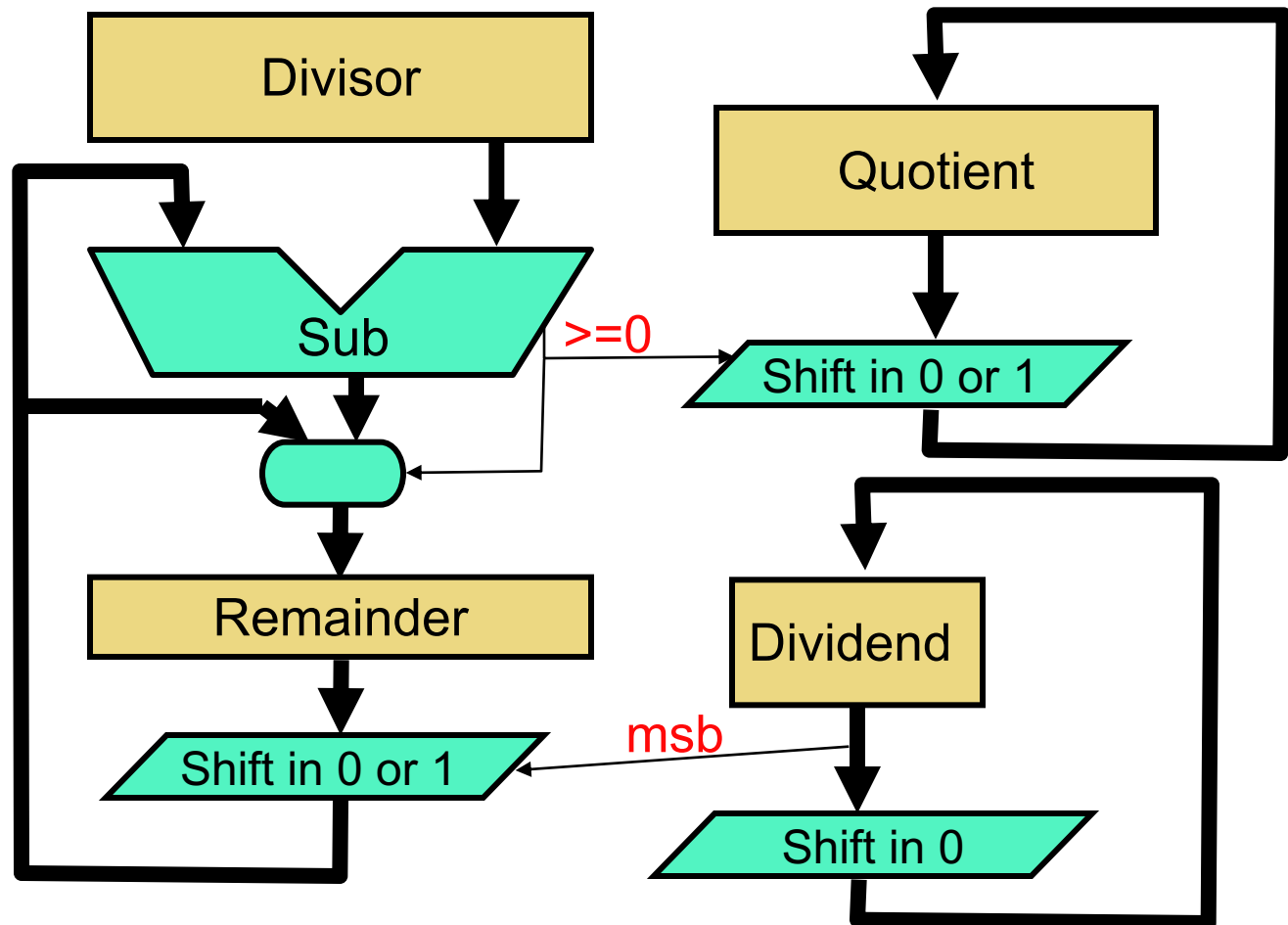

- N cycles for n-bit divide



# Fast Addition

# Theme: Hardware $\neq$ Software


---

- Hardware can do things that software fundamentally can't
  - And vice versa (of course)
- In hardware, it's easier to trade **resources** for **latency**
- One example of this: **speculation**
  - Slow computation waiting for some slow input?
  - Input one of two things?
  - **Compute with both (slow), choose right one later (fast)**
- Does this make sense in software? Not on a single core
- Difference? hardware is parallel, software is sequential
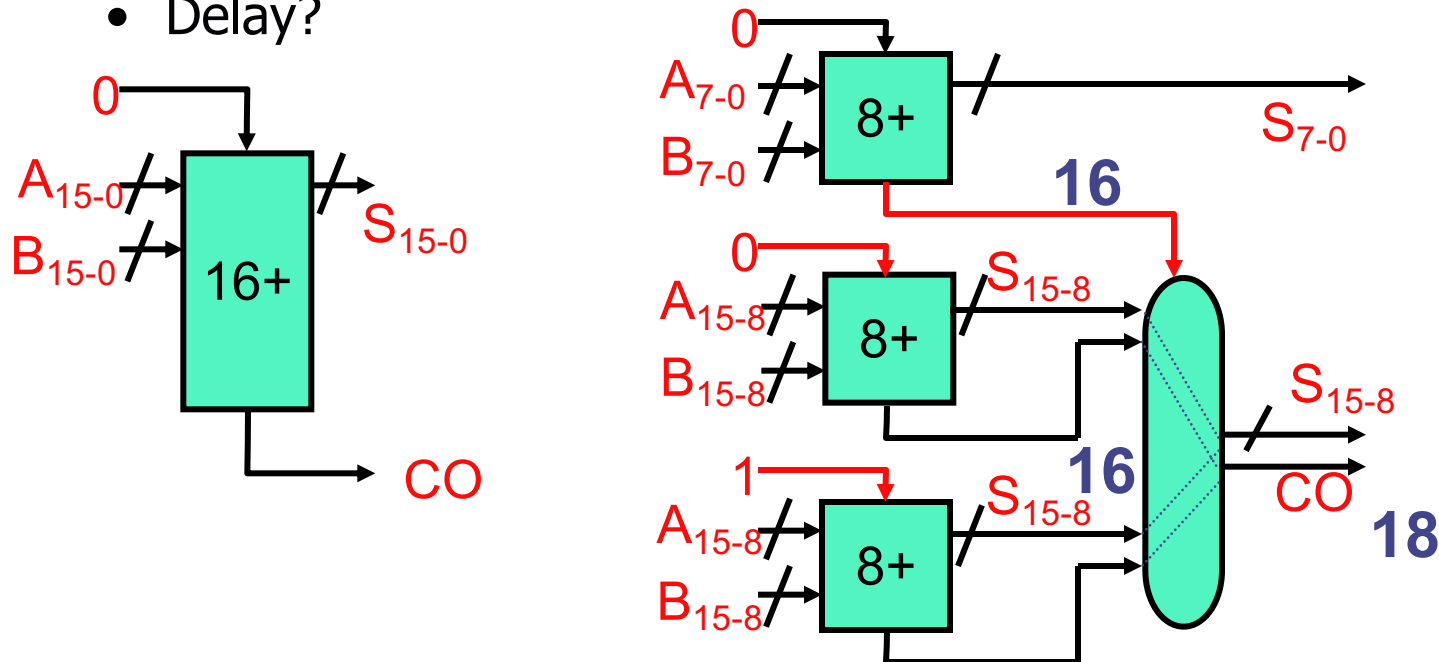
# Carry-Select Adder


- **Carry-select adder**

- Do  $A_{15-8} + B_{15-8}$  twice, once assuming  $C_8$  ( $CO_7$ ) = 0, once = 1
- Choose the correct one when  $CO_7$  finally becomes available
- + Effectively cuts carry chain in half (break critical path)
- Extra mux increases delay
- Delay?


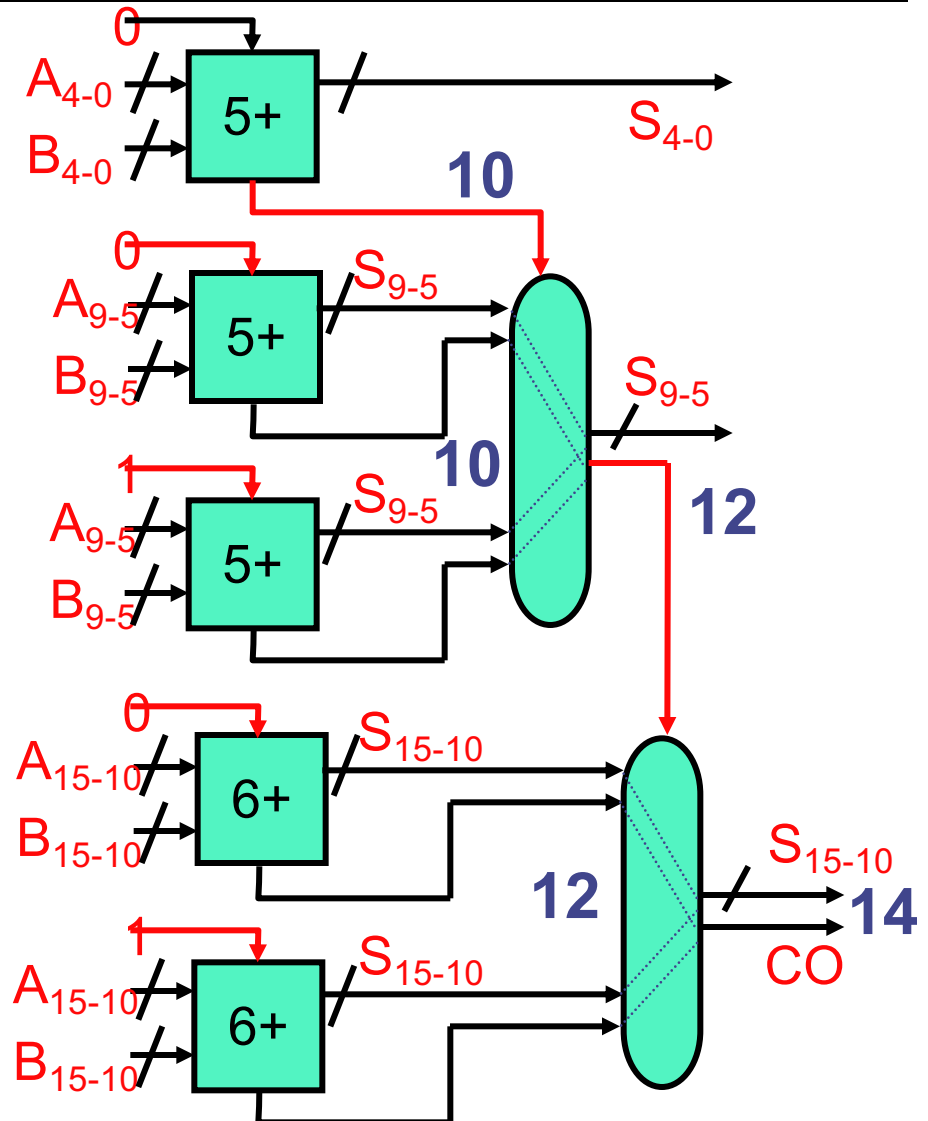
# Multi-Segment Carry-Select Adder

- Multiple segments
  - Example: 5, 5, 6 bit = 16 bit
- Hardware cost
  - Still mostly linear ( $\sim 2x$ )
  - Compute each segment with 0 and 1 carry-in
  - Serial mux chain
- Delay
  - 5-bit adder (10) + Two muxes (4) = 14




# Carry-Select Adder Delay

---

- What is **two segment** carry-select adder delay?
  - $d(CO_{15}) = \text{MAX}(d(CO_{15-8}), d(CO_{7-0})) + 2$
  - $d(CO_{15}) = \text{MAX}(2*8, 2*8) + 2 = \mathbf{18}$
  - In general:  $\mathbf{2*(N/2) + 2 = N+2}$  (vs  $\mathbf{2N}$  for RCA)
- What about **four equal segments**?
  - Would it be  $2*(N/4) + 2 = 10$ ? Not quite
  - $d(CO_{15}) = \text{MAX}(d(CO_{15-12}), d(CO_{11-0})) + 2$
  - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(d(CO_{11-8}), d(CO_{7-0})) + 2) + 2$
  - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(d(CO_{7-4}), d(CO_{3-0})) + 2) + 2) + 2$
  - $d(CO_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(2*4, 2*4) + 2) + 2) + 2$
  - $d(CO_{15}) = 2*4 + 3*2 = \mathbf{14}$
- N-bit adder in M equal pieces:  $\mathbf{2*(N/M) + (M-1)*2}$ 
  - 16-bit adder in 8 parts:  $2*(16/8) + 7*2 = \mathbf{18}$

# 16b Carry-Select Adder Delay

 


# Another Option: Carry Lookahead

---

- Is carry-select adder as fast as we can go?
  - Nope!
- Another approach to using additional resources
  - Instead of redundantly computing sums assuming different carries
  - Use redundancy to compute carries more quickly
    - This approach is called **carry lookahead (CLA)**

# A & B → Generate & Propagate

- Let's look at the single-bit carry-out function
  - $CO = AB|AC|BC$
  - Factor out terms that use only A and B (available immediately)
  - $CO = (AB)|(A|B)C$
  - $(AB)$ : generates carry-out regardless of incoming C → rename to **G**
  - $(A|B)$ : propagates incoming C → rename to **P**
  - $CO = G|PC$

 



# Infinite Hardware CLA

---

- Can expand  $C_{1...N}$  in terms of  $G$ 's,  $P$ 's, and  $C_0$ 
  - Example:  $C_{16}$ 
    - $C_{16} = G_{15} \mid P_{15}C_{15}$
    - $C_{16} = G_{15} \mid P_{15}(G_{14} \mid P_{14}C_{14})$
    - $C_{16} = G_{15} \mid P_{15}G_{14} \mid \dots \mid P_{15}P_{14}\dots P_2P_1G_0 \mid P_{15}P_{14}\dots P_2P_1C_0$
  - Similar expansions for  $C_{15}$ ,  $C_{14}$ , etc.
- How much does this cost?
  - $C_N$  needs:  $N$  AND's + 1 OR's, largest have  $N+1$  inputs
  - $C_N \dots C_1$  needs:  **$N*(N+1)/2$**  AND's +  **$N$**  OR's, max  $N+1$  inputs
  - $N=16$ : 152 total gates, max input 17
  - $N=64$ : 2144 total gates, max input 65
- And how fast is it really?
  - Not that fast, unfortunately, 17-input gates are really slow

## 3b Infinite CLA example

---


# Compromise: Multi-Level CLA

---

- **Ripple carry**
  - + Few small gates:  $5N$  gates, max 3 inputs
  - Laid in series:  $2N$  (linear) latency
- **Infinite hardware CLA**
  - Many big gates:  $N*(N+3)/2$  additional gates, max  $N+1$  inputs
  - + Laid in parallel: constant 4 latency
- Is there a compromise?
  - Reasonable number of small gates?
  - Sublinear (doesn't have to be constant) latency?
  - **Yes, multi-level CLA**: exploits hierarchy to achieve this
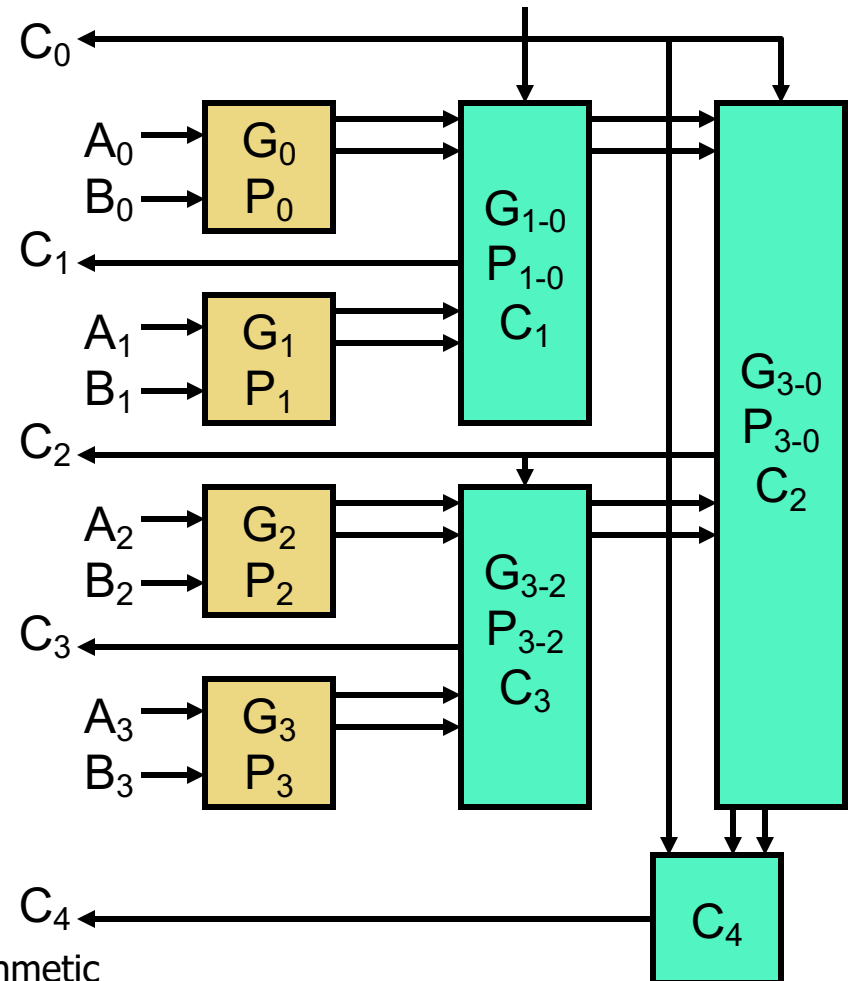
# Carry Lookahead Adder (CLA)

- Calculate “propagate” and “generate” based on A, B
  - Not based on carry in
- Combine with tree structure
- High-level idea
  - **Tree gives logarithmic delay**
  - Reasonable area



# Individual G & P → Windowed G & P

---

- **Windowed G/P**: useful abstraction for multi-level CLA
- Individual carry equations
  - $C_1 = G_0 \mid P_0C_0$ ,  $C_2 = G_1 \mid P_1C_1$
- Infinite hardware CLA equations
  - $C_1 = G_0 \mid P_0C_0$
  - $C_2 = G_1 \mid P_1G_0 \mid P_1P_0C_0$
- Group terms into “windows”
  - $C_2 = (G_1 \mid P_1G_0) \mid (P_1P_0)C_0$
  - $C_2 = G_{1-0} \mid P_{1-0}C_0$
- $G_{1-0}$ ,  $P_{1-0}$  are window G & P
  - a single bit summarizing information from all the bits in the window
  - $G_{1-0}$ : carry-out generated by bits [1:0]
  - $P_{1-0}$ : carry-out propagated by bits [1:0]
    - would a carry-in to the start of the window create a carry-out?

# 3b Windowed G&P Example

---


# Two-Level CLA for 4-bit Adder

---

- Individual carry equations
  - $C_1 = G_0 \mid P_0C_0$ ,  $C_2 = G_1 \mid P_1C_1$ ,  $C_3 = G_2 \mid P_2C_2$ ,  $C_4 = G_3 \mid P_3C_3$
- Infinite hardware CLA equations
  - $C_1 = G_0 \mid P_0C_0$
  - $C_2 = G_1 \mid P_1G_0 \mid P_1P_0C_0$
  - $C_3 = G_2 \mid P_2G_1 \mid P_2P_1G_0 \mid P_2P_1P_0C_0$
  - $C_4 = G_3 \mid P_3G_2 \mid P_3P_2G_1 \mid P_3P_2P_1G_0 \mid P_3P_2P_1P_0C_0$
- Hierarchical CLA equations
  - **First level:** expand  $C_2$  using  $C_1$ ,  $C_4$  using  $C_3$ 
    - $C_2 = G_1 \mid P_1(G_0 \mid P_0C_0) = (G_1 \mid P_1G_0) \mid (P_1P_0)C_0 = G_{1-0} \mid P_{1-0}C_0$
    - $C_4 = G_3 \mid P_3(G_2 \mid P_2C_2) = (G_3 \mid P_3G_2) \mid (P_3P_2)C_2 = G_{3-2} \mid P_{3-2}C_2$
  - **Second level:** expand  $C_4$  using expanded  $C_2$ 
    - $C_4 = G_{3-2} \mid P_{3-2}(G_{1-0} \mid P_{1-0}C_0) = (G_{3-2} \mid P_{3-2}G_{1-0}) \mid (P_{3-2}P_{1-0})C_0$
    - $C_4 = G_{3-0} \mid P_{3-0}C_0$
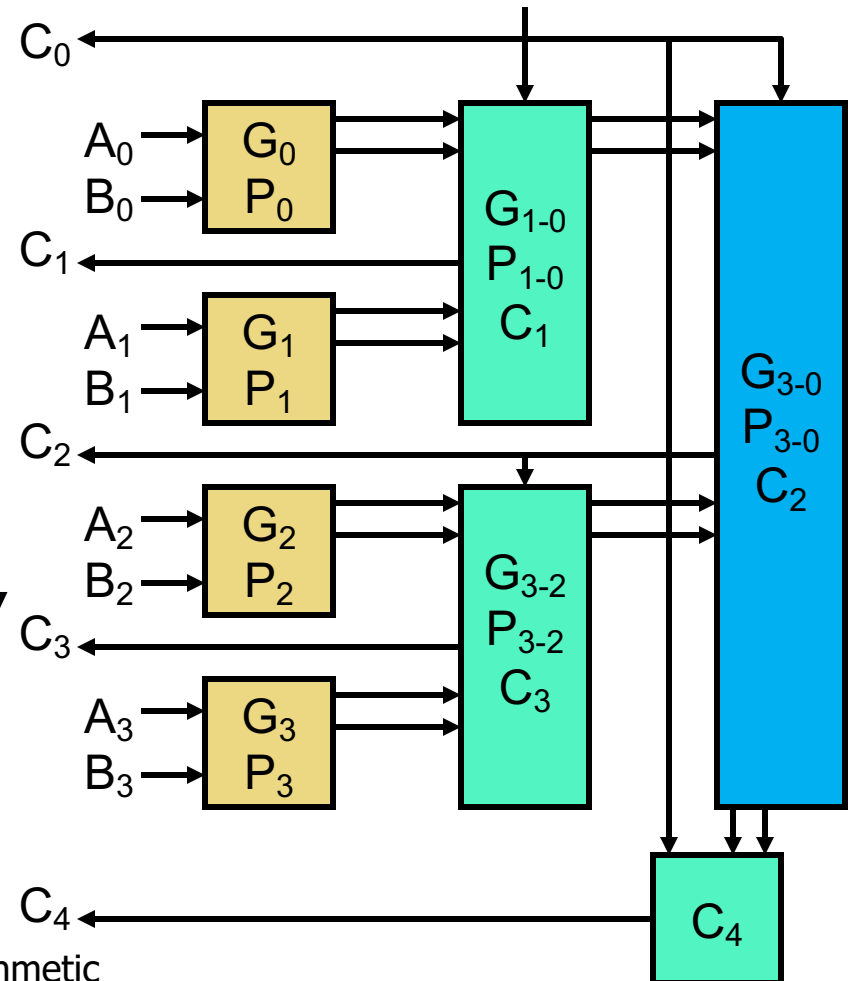
# Two-Level CLA for 4-bit Adder


- **Top first-level CLA block**
  - Input:  $C_0, G_0, P_0, G_1, P_1$
  - Output:  $C_1, G_{1-0}, P_{1-0}$
- **Bottom first-level CLA block**
  - Input:  $C_2, G_2, P_2, G_3, P_3$
  - Output:  $C_3, G_{3-2}, P_{3-2}$
- **Second-level CLA block**
  - Input:  $C_0, G_{1-0}, P_{1-0}, G_{3-2}, P_{3-2}$
  - Output:  $C_2, G_{3-0}, P_{3-0}$
- These 3 blocks are “the same”
- $C_4$  block
  - Input:  $C_0, G_{3-0}, P_{3-0}$
  - Output:  $C_4$





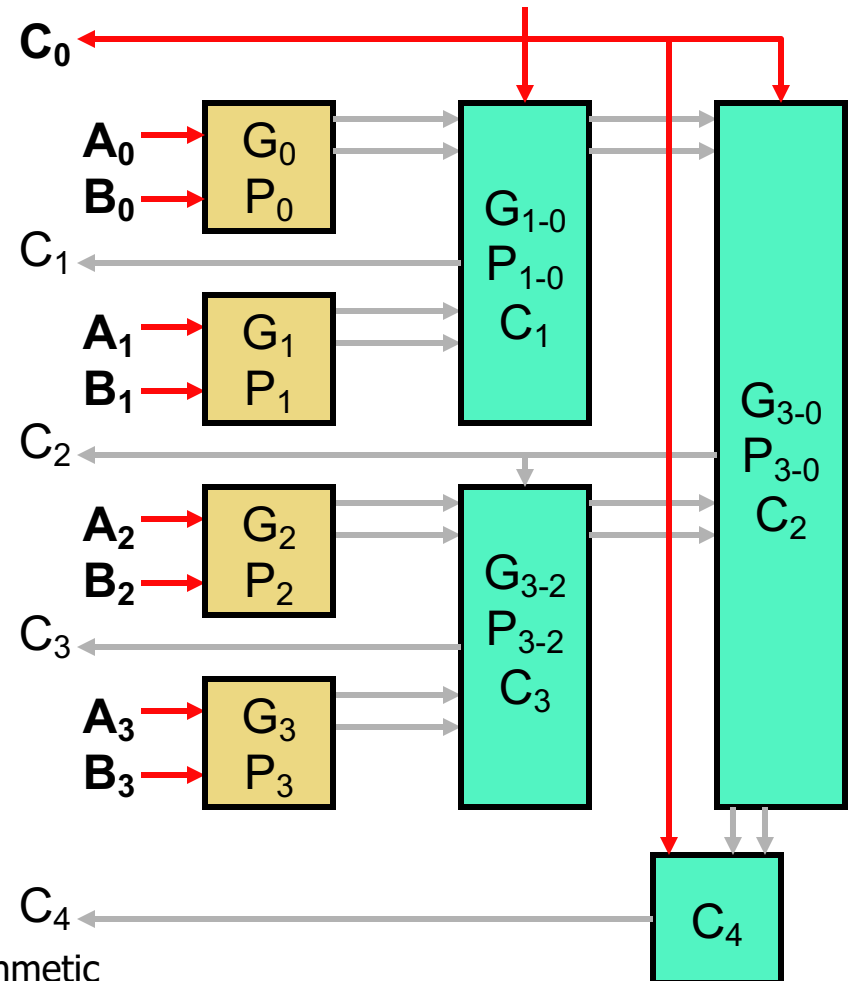
# 4-bit CLA Timing: d0

- Which signals are ready at 0 gate delays (d0)?
  - $C_0$
  - $A_0, B_0$
  - $A_1, B_1$
  - $A_2, B_2$
  - $A_3, B_3$



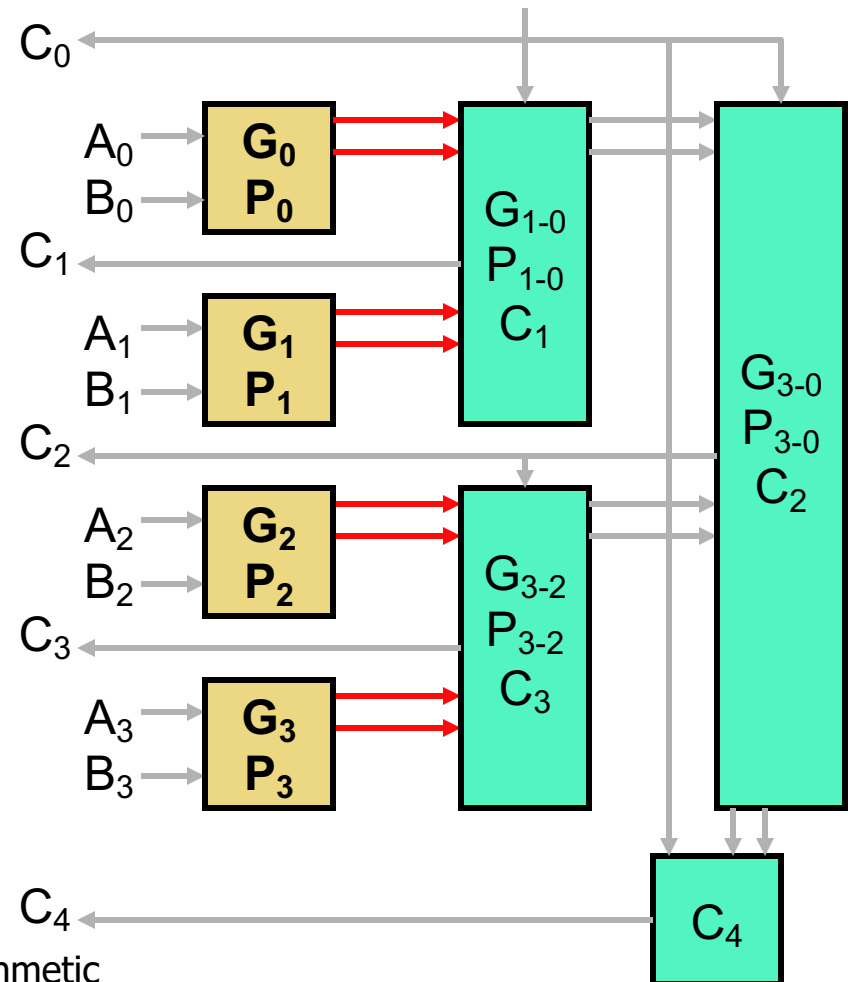
# 4-bit CLA Timing: d1

- Signals ready from before
  - d0:  $C_0$ ,  $A_i$ ,  $B_i$
- New signals ready at d1
  - $P_0 = A_0 \mid B_0$ ,  $G_0 = A_0 B_0$
  - $P_1 = A_1 \mid B_1$ ,  $G_1 = A_1 B_1$
  - $P_2 = A_2 \mid B_2$ ,  $G_2 = A_2 B_2$
  - $P_3 = A_3 \mid B_3$ ,  $G_3 = A_3 B_3$



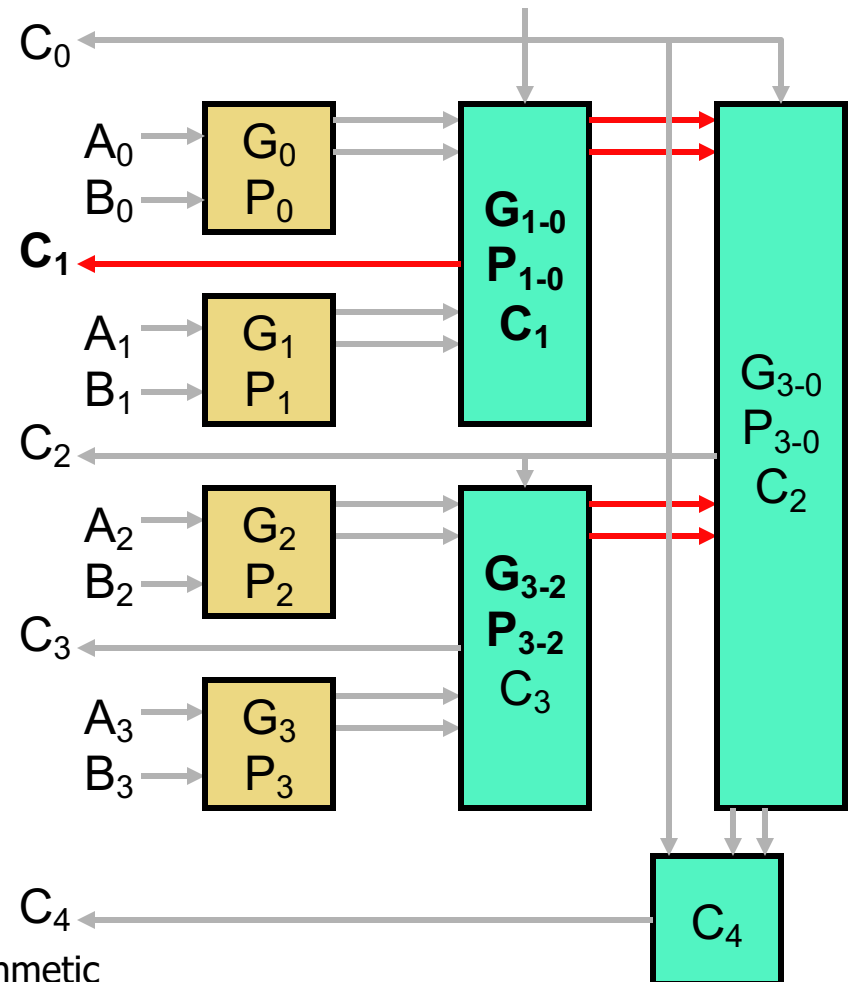
# 4-bit CLA Timing: d3

- Signals ready from before
  - d0:  $C_0$ ,  $A_i$ ,  $B_i$
  - d1:  $P_i$ ,  $G_i$
- New signals ready at d3
  - $P_{1-0} = P_1 P_0$
  - $G_{1-0} = G_1 \mid P_1 G_0$
  - $C_1 = G_0 \mid P_0 C_0$
  - $P_{3-2} = P_3 P_2$
  - $G_{3-2} = G_3 \mid P_3 G_2$
  - $C_3$  is not ready



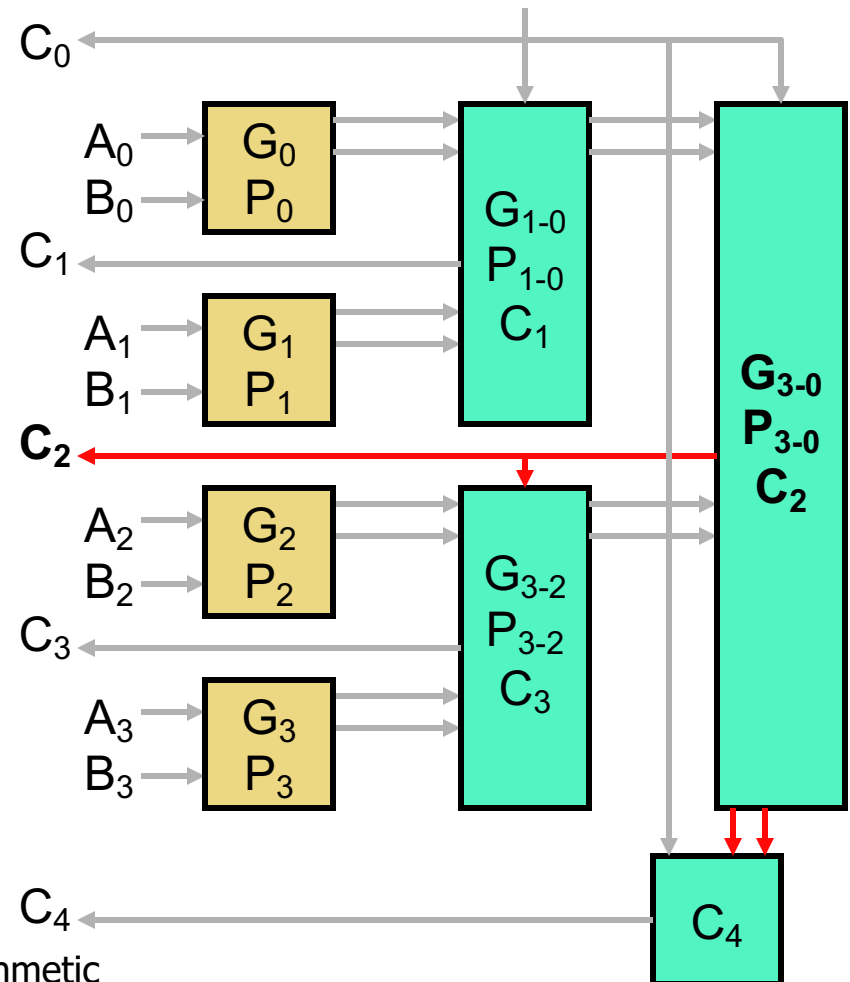
# 4-bit CLA Timing: d5

- Signals ready from before
  - d0:  $C_0, A_i, B_i$
  - d1:  $P_i, G_i$
  - d3:  $P_{1-0}, G_{1-0}, C_1, P_{3-2}, G_{3-2}$
- New signals ready at d5
  - $P_{3-0} = P_{3-2} P_{1-0}$
  - $G_{3-0} = G_{3-2} \mid P_{3-2} G_{1-0}$
  - $C_2 = G_{1-0} \mid P_{1-0} C_0$



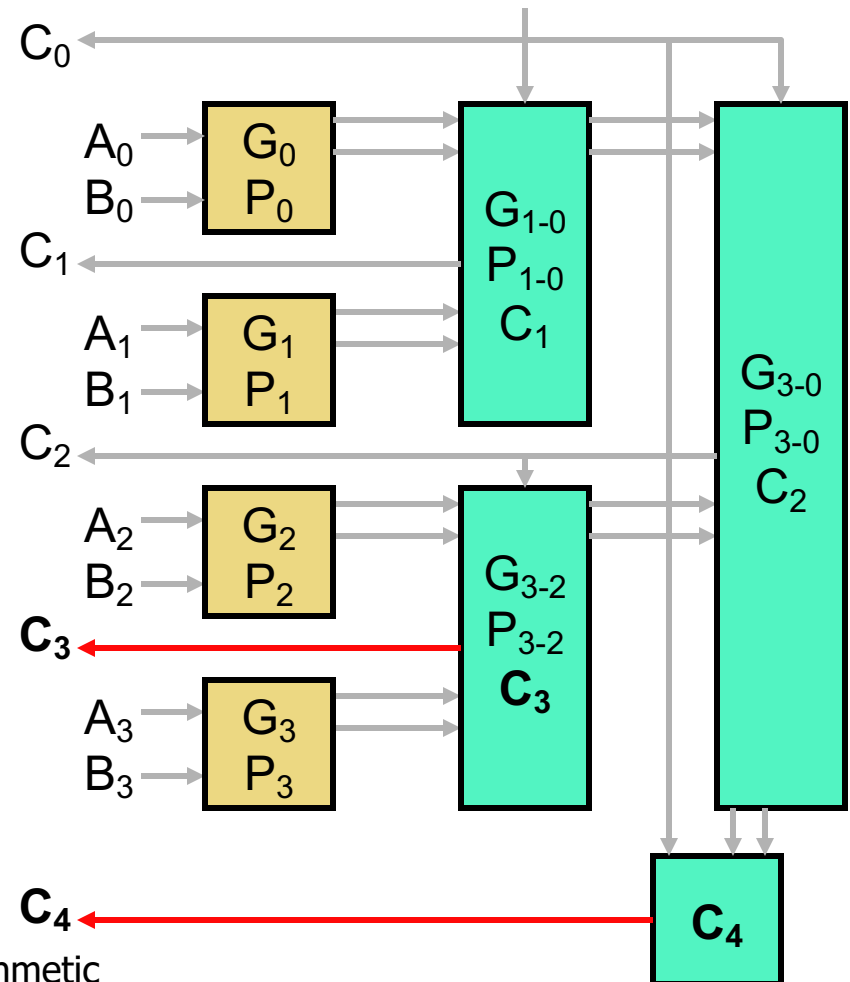
# 4-bit CLA Timing: d7

- Signals ready from before
  - d0:  $C_0$ ,  $A_i$ ,  $B_i$
  - d1:  $P_i$ ,  $G_i$
  - d3:  $P_{1-0}$ ,  $G_{1-0}$ ,  $C_1$ ,  $P_{3-2}$ ,  $G_{3-2}$
  - d5:  $P_{3-0}$ ,  $G_{3-0}$ ,  $C_2$
- New signals ready at d7
  - $C_3 = G_2 \mid P_2 C_2$
  - $C_4 = G_{3-0} \mid P_{3-0} C_0$
- $S_i$  ready d1 after  $C_i$



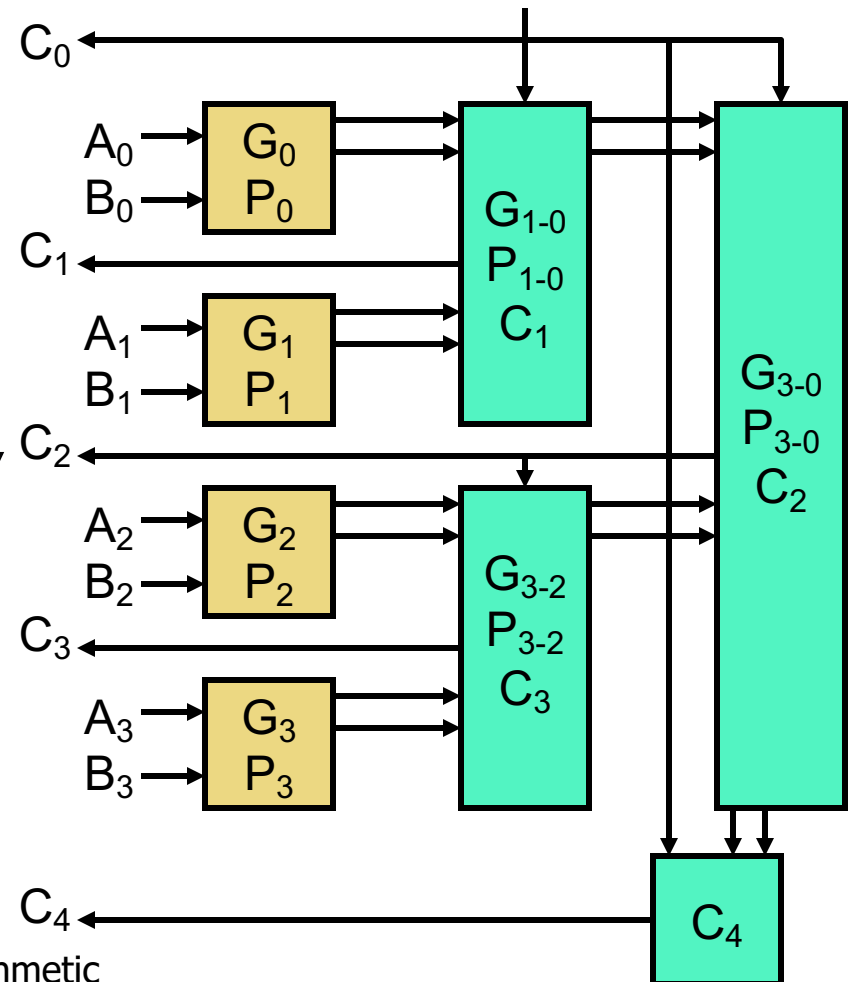
# Two-Level CLA for 4-bit Adder

- Size?
  - CLA blocks: 5 gates, max 3 inputs (akin to infinite CLA with  $N=2$ )
    - 3 of these
  - $C_4$  block: 2 gates, max 2 inputs
  - Total: **17 gates, max 3 inputs**
    - Infinite: 14, 5
- Latency?
  - 2 for "top" CLA, 4 for "first-level"
    - G/P go "up", C go "down"
  - Total: **8** (7 for CLA, 1 for sum)
    - Infinite: 4
- 2L is bigger **and** slower ☹️



 
# Two-Level CLA for 16-bit Adder

- 4 G/P inputs per level
- Hardware?
  - First level: 14 gates \* 4 blocks
  - Second level: 14 gates \* 1 block
  - $C_{16}$  block: 2 gates
  - Total: **72 gates**
    - largest gate: **4 inputs**
    - Infinite: 152 gates, 17 inputs
- Latency?
  - Total: **8** (1 + 2 + 2 + 2 + 1)
  - Infinite: 4 (1 + 2 + 1)
- CLA for a 64-bit adder?


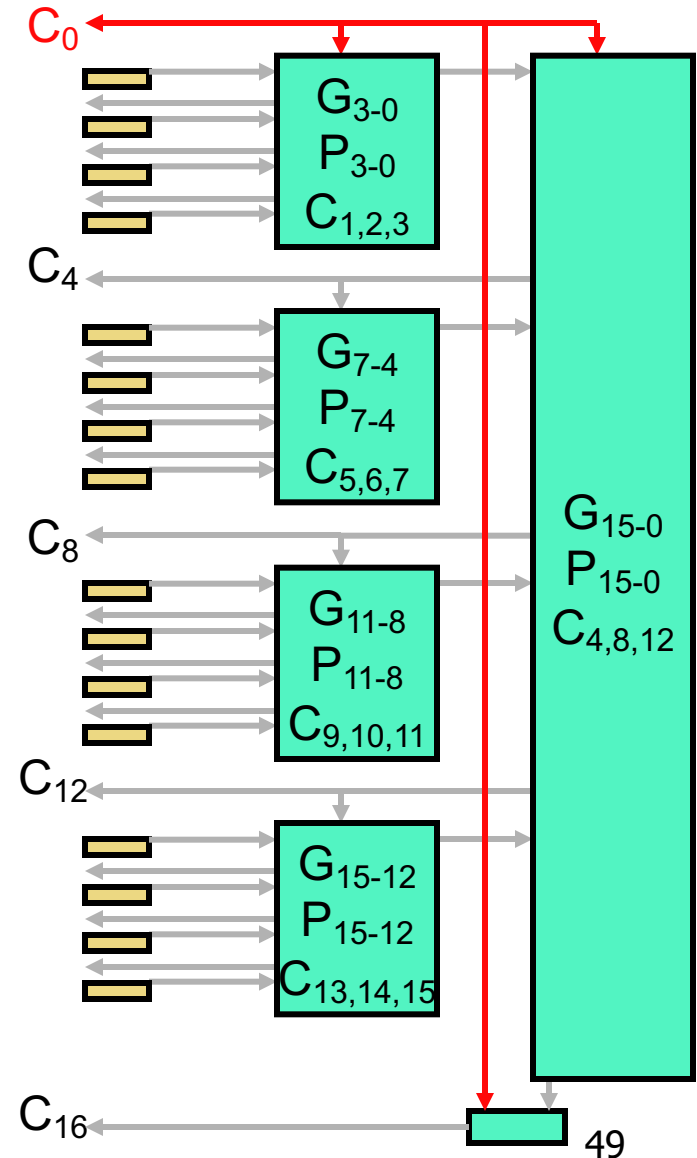
# 16-bit CLA Timing: d0


- What is ready after **0** gate delays?
  - $C_0$





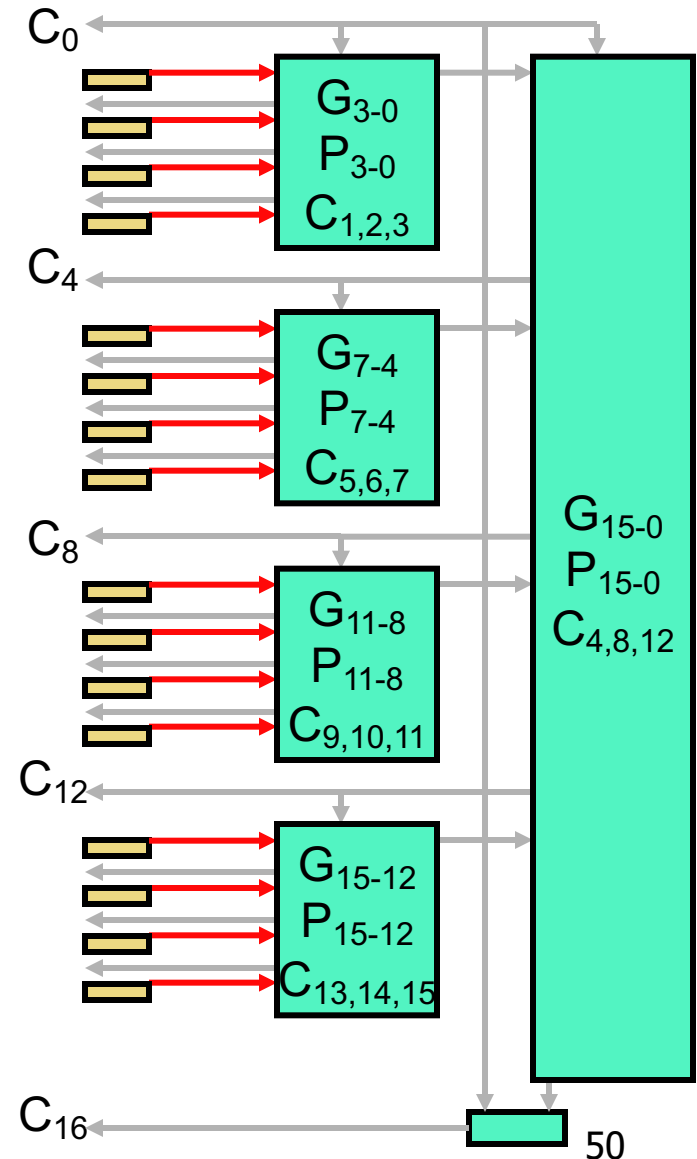
# 16-bit CLA Timing: d1

- What is ready after **1** gate delay?
  - Individual G/P



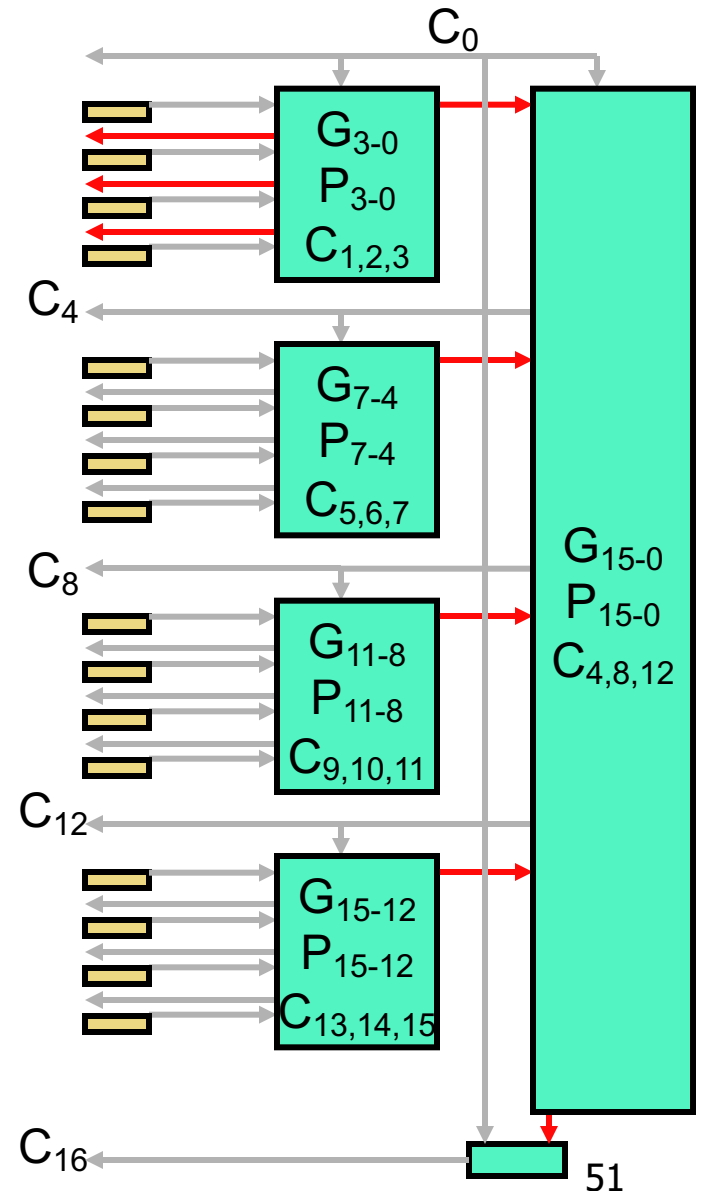
# 16-bit CLA Timing: d3

- What is ready after **3** gate delays?
  - 1<sup>st</sup> level group G/P
  - Interior carries of 1<sup>st</sup> group
    - $C_1, C_2, C_3$



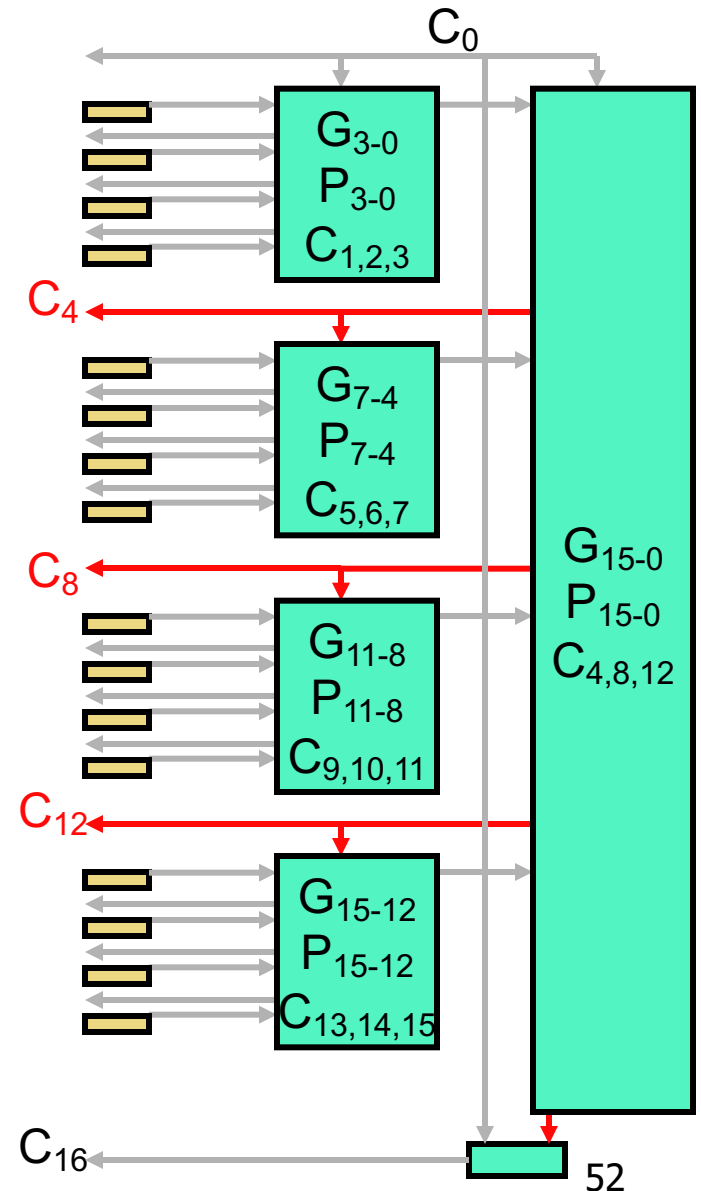
# 16-bit CLA Timing: d5

- And after **5** gate delays?
  - Outer level group G/P
  - Outer level “interior” carries
    - $C_4, C_8, C_{12}$


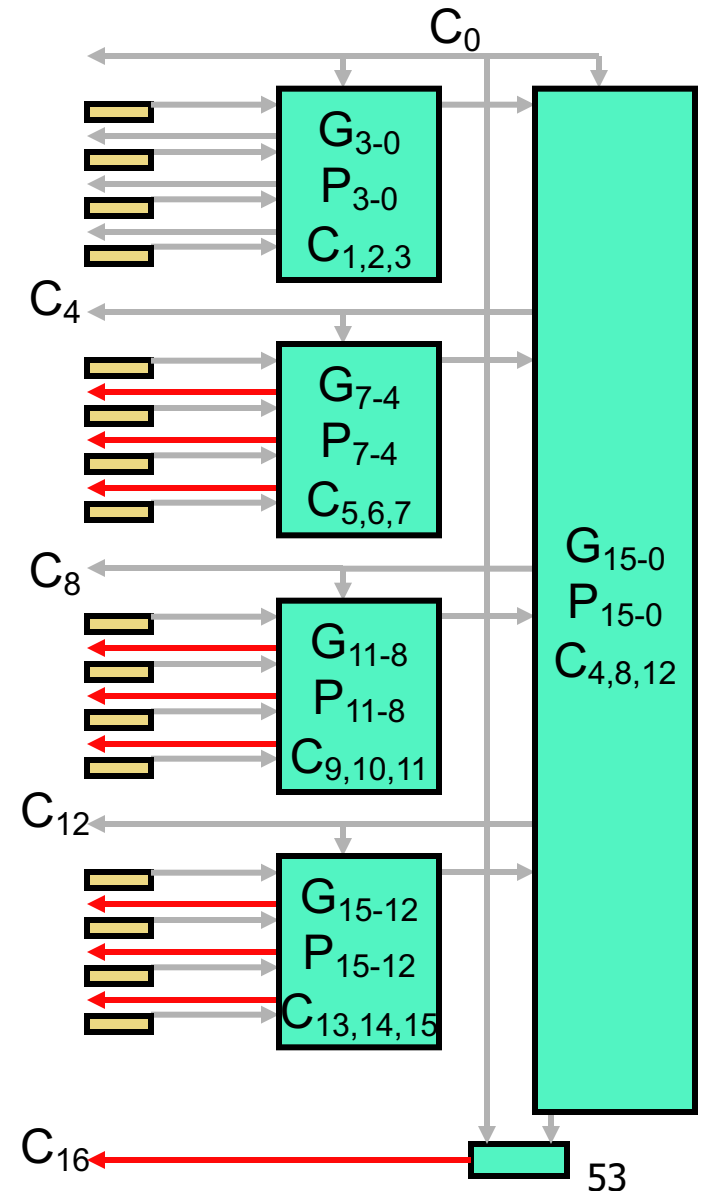
# 16-bit CLA Timing: d7


- And after **7** gate delays?
  - $C_{16}$
  - First level "interior" carries
    - $C_5, C_6, C_7$
    - $C_9, C_{10}, C_{11}$
    - $C_{13}, C_{14}, C_{15}$
  - Essentially, all remaining carries
- $S_i$  ready 1 gate delay after  $C_i$ 
  - All sum bits ready after 8 delays!
  - Same as 2-level 4-bit CLA
  - All 2-level CLAs have similar delay structure



# Adders In Real Processors

---

- Real processors super-optimize their adders
  - Ten or so different versions of CLA
  - Highly optimized versions of carry-select
  - Other gate techniques: carry-skip, conditional-sum
  - Sub-gate (transistor) techniques: Manchester carry chain
  - Combinations of different techniques
    - Alpha 21264 used CLA+CSelA+RippleCA
    - Used at different levels
- Even more optimizations for incrementers
  - Why?

 

**FIG 10.47** Area vs. delay of synthesized adders

# Shifts & Rotates

# Shift and Rotation Instructions

---

- Left/right shifts are useful...
  - Fast multiplication/division by small constants (next)
  - Bit manipulation: extracting and setting individual bits in words
- Right shifts
  - Can be **logical** (shift in 0s) or **arithmetic** (shift in copies of MSB)
    - `sr1 110011, 2 = 001100`
    - `sra 110011, 2 = 111100`
  - Caveat: for negative numbers, `sra` is **not** equal to division by 2
    - Consider:  $-1 / 16 = ?$
- Rotations are less useful...
  - But almost “free” if shifter is there
  - MIPS and LC4 have only shifts, x86 has shifts and rotations



# Compiler Opt: Strength Reduction

---

- **Strength reduction**: compilers will do this (sort of)

$$A * 4 = A \ll 2$$

$$A * 5 = (A \ll 2) + A$$

$$A / 8 = A \gg 3 \quad (\text{only if } A \text{ is unsigned})$$




- Useful for address calculation: all basic data types are  $2^M$  in size

```
int A[100];
```

$$\&A[N] = A + (N * \text{sizeof}(\text{int})) = A + N * 4 = A + N \ll 2$$

   
# A Simple Shifter

- The simplest 16-bit shifter: can only shift left by 1
  - **Implement using wires (no logic!)**
- Slightly more complicated: can shift left by 1 or 0
  - Implement using wires and a multiplexor (mux16\_2to1)


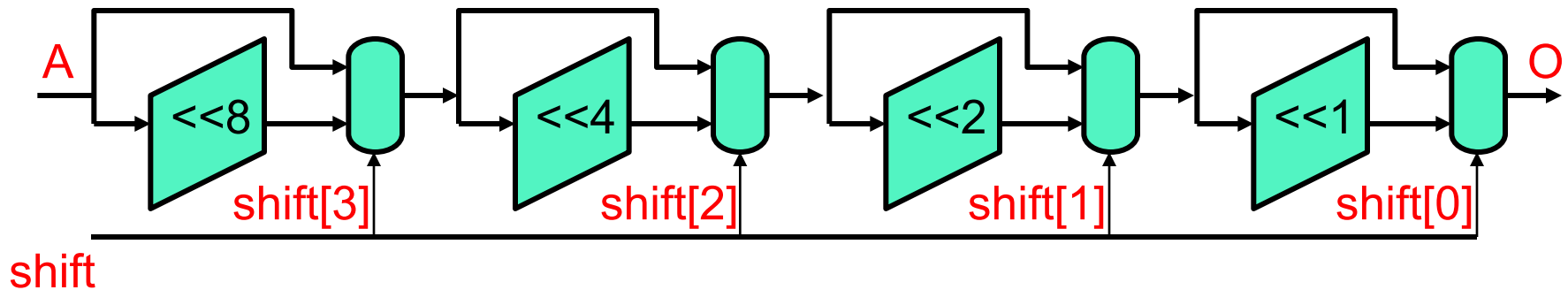
# Barrel Shifter

- What about shifting left by any amount 0–15?
- 16 consecutive “left-shift-by-1-or-0” blocks?
  - Would take too long (how long?)
- **Barrel shifter**: 4 “shift-left-by-X-or-0” blocks ( $X = 1, 2, 4, 8$ )
  - What is the delay?



- Similar barrel designs for right shifts and rotations

# Shifter in Verilog

---

- Logical shift operators << >>

- performs zero-extension for >>

```
wire [15:0] a = b << c[3:0];
```

- Arithmetic shift operator >>>

- performs sign-extension
- requires a signed wire input

```
wire signed [15:0] b;
```

```
wire [15:0] a = b >>> c[3:0];
```

# Multiplication

# 3rd Grade: Decimal Multiplication

---

$$\begin{array}{r} 19 \quad // \text{ multiplicand} \\ * 12 \quad // \text{ multiplier} \\ \hline 38 \\ + 190 \\ \hline 228 \quad // \text{ product} \end{array}$$

- Start with product 0, repeat steps until no multiplier digits
  - Multiply multiplicand by least significant multiplier digit
  - Add to product
  - Shift multiplicand one digit to the left (multiply by 10)
  - Shift multiplier one digit to the right (divide by 10)
- Product of N-digit and M-digit numbers may have N+M digits

# Binary Multiplication: Same Refrain

---

|       |       |                |                 |
|-------|-------|----------------|-----------------|
|       | 19 =  | 010011         | // multiplicand |
| *     | 12 =  | 001100         | // multiplier   |
| <hr/> |       |                |                 |
|       | 0 =   | 00000000000000 |                 |
|       | 0 =   | 00000000000000 |                 |
|       | 76 =  | 000001001100   |                 |
|       | 152 = | 000010011000   |                 |
|       | 0 =   | 00000000000000 |                 |
| +     | 0 =   | 00000000000000 |                 |
| <hr/> |       |                |                 |
|       | 228 = | 000011100100   | // product      |

± Smaller base → more steps, each is simpler

- Multiply multiplicand by **least significant multiplier digit**  
+ 0 or 1 → no actual multiplication, add multiplicand or not
- Add to total: we know how to do that
- Shift multiplicand left, multiplier right by one digit

# Software Multiplication


---

- Can implement this algorithm in software
- Inputs: `md` (multiplicand) and `mr` (multiplier)

```
int pd = 0;    // product
int i = 0;
for (i = 0; i < 16 && mr != 0; i++) {
    if (mr & 1) {
        pd = pd + md;
    }
    md = md << 1;    // shift left
    mr = mr >> 1;    // shift right
}
```




# Hardware Multiply: Sequential

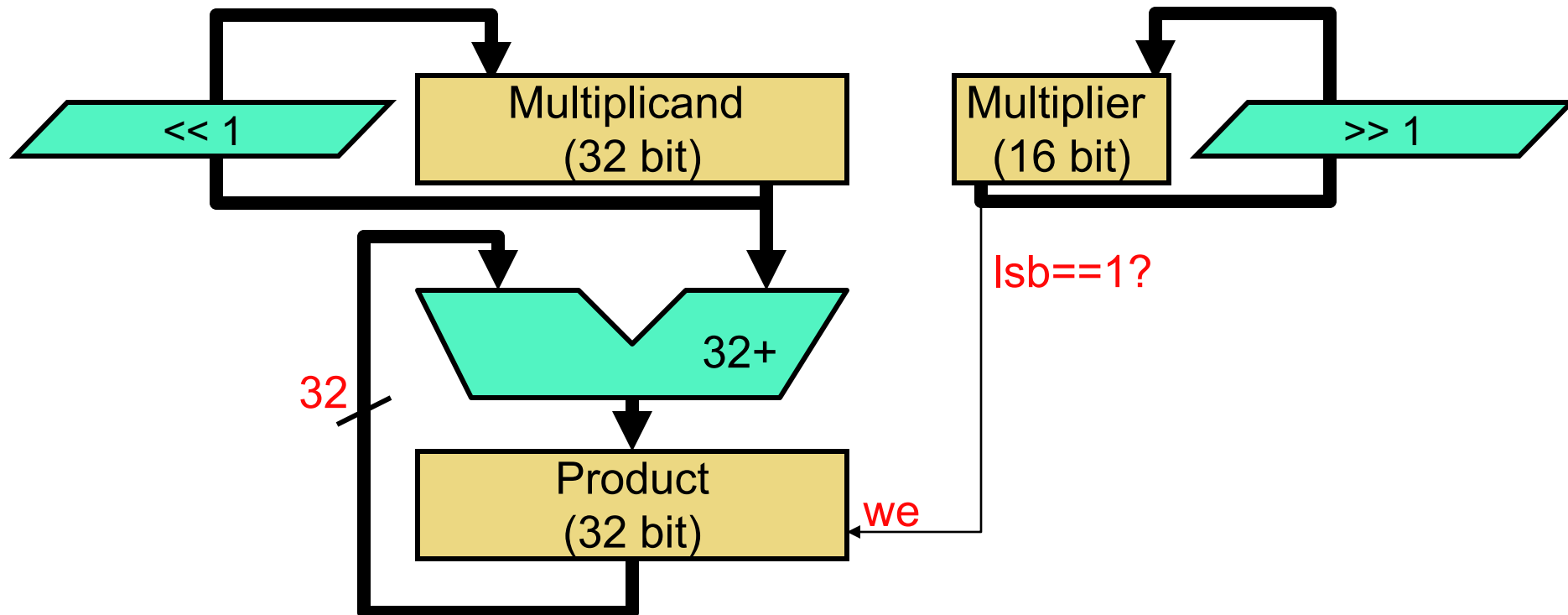

- **Control:** repeat 16 times
  - If least significant bit of multiplier is 1...
    - Then add multiplicand to product
  - Shift multiplicand left by 1
  - Shift multiplier right by 1

# Hardware Multiply: Combinational

 

- Multiply by N bits at a time using N adders
  - Example: N=5, terms (P=product, C=multiplicand, M=multiplier)
  - $P = (M[0] ? (C) : 0) + (M[1] ? (C \ll 1) : 0) + (M[2] ? (C \ll 2) : 0) + (M[3] ? (C \ll 3) : 0) + \dots$
  - Arrange like a tree to reduce gate delay critical path
- Delay?  $N^2$  vs  $N \cdot \log N$ ? Not that simple, depends on adder
  - Approx " $2N$ " versus " $N + \log N$ ", with optimization:  $O(\log N)$

# Partial Sums/Carries

---

- Observe: carry-outs don't have to be chained immediately

- Can be saved for later and added back in

$$00111 = 7$$

$$\underline{+00011} = 3$$

$$00100 \quad // \text{ partial sums (sums without carries)}$$

$$\underline{+00110} \quad // \text{ partial carries (carries without sums)}$$

$$01010 = 10$$

- Partial sums/carries use simple half-adders, not full-adders
  - + Aren't "chained" → can be done in two levels of logic
  - Must sum partial sums/carries eventually, and this sum is chained
    - $d(\text{CS-adder}) = 2 + d(\text{normal-adder})$
  - What is the point?

# Three Input Addition

---

- Observe: only 0/1 carry-out possible even if 3 bits added

$$00111 = 7$$

$$00011 = 3$$

$$\underline{+00010} = 2$$

$$00110 \quad // \text{ partial sums (sums without carries)}$$

$$\underline{+00110} \quad // \text{ partial carries (carries without sums)}$$

$$01100 = 12$$

- Partial sums/carries use full adders
- + Still aren't "chained" → can be done in two levels of logic
- The point is  $\text{delay}(\text{CS-adder}) = 2 + \text{delay}(\text{normal-adder})...$
- ...even for adding 3 numbers!
- $2 + \text{delay}(\text{normal-adder}) < 2 * \text{delay}(\text{normal-adder})$

# Hardware != Software: Part Deux

---


- Recall: hardware is parallel, software is sequential
- Exploit: evaluate independent sub-expressions in parallel
- Example I:  $S = A + B + C + D$ 
  - Software? 3 steps: (1)  $S1 = A+B$ , (2)  $S2 = S1+C$ , (3)  $S = S2+D$
  - + Hardware? 2 steps: (1)  $S1 = A+B$ ,  $S2=C+D$ , (2)  $S = S1+S2$
- Example II:  $S = A + B + C$ 
  - Software? 2 steps: (1)  $S1 = A+B$ , (2)  $S = S1+C$
  - Hardware? 2 steps: (1)  $S1 = A+B$  (2)  $S = S1+C$
  - + Actually hardware can do this in 1.2 steps! (CSA adder)

# Carry Save Addition (CSA)


---

- **Carry save addition (CSA):**  $\text{delay}(N \text{ adds}) < N * d(1 \text{ add})$ 
  - Enabling observation: unconventional view of full adder
    - 3 inputs  $(A, B, C_{in}) \rightarrow 2$  outputs  $(S, C_{out})$
  - If adding two numbers, only thing to do is chain  $C_{out}$  to  $C_{in+1}$ 
    - But what if we are adding three numbers  $(A+B+D)$ ?
  - One option: back-to-back conventional adders
    - $(A, B, C_{inT}) \rightarrow (T, C_{outT})$ , chain  $C_{outT}$  to  $C_{inT+1}$
    - $(T, D, C_{inS}) \rightarrow (S, C_{outS})$ , chain  $C_{outS}$  to  $C_{inS+1}$
  - Notice: we have **three independent inputs** to feed first adder
    - $(A, B, D) \rightarrow (T, C_{outT})$ , **no chaining (CSA: 2 gate levels)**
      - $T$ :  $A+B+D$  (the **partial sum**)
      - $C_{outT}$ :  $A+BD$  (the **partial carry**)
    - $(T, C_{outT}, C_{inS}) \rightarrow (S, C_{outS})$ , chain  $C_{outS}$  to  $C_{inS+1}$

# Carry Save Addition (CSA)


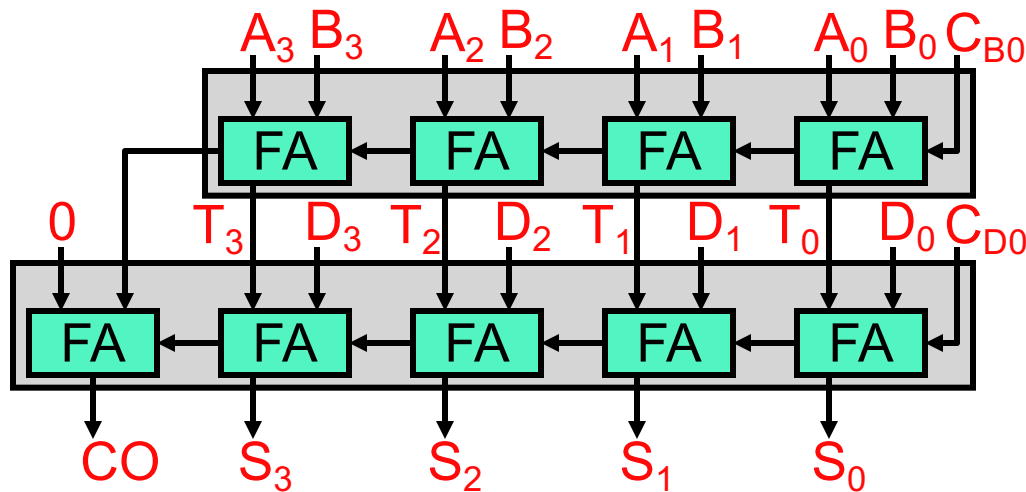


- 2 RC adders

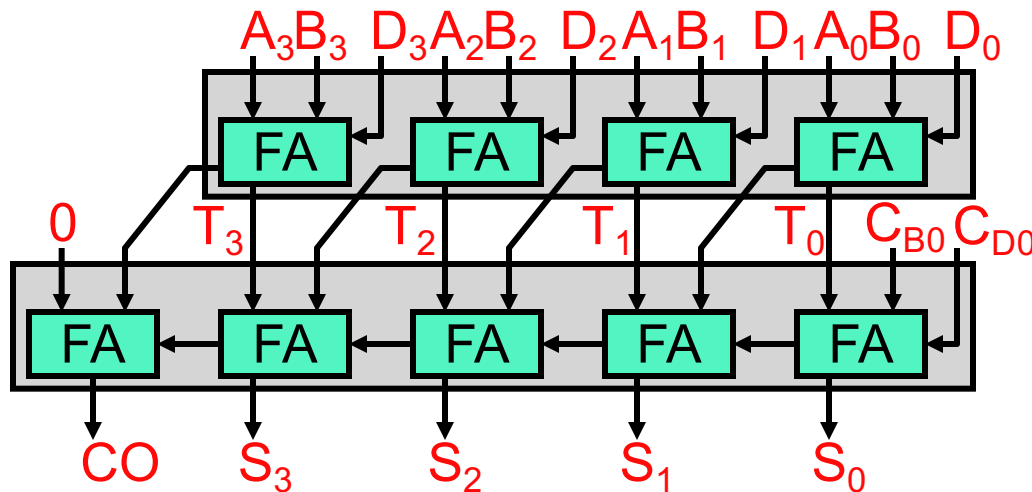

- CSA+RC adder
  - Subtraction works too


# Carry Save Addition Delay

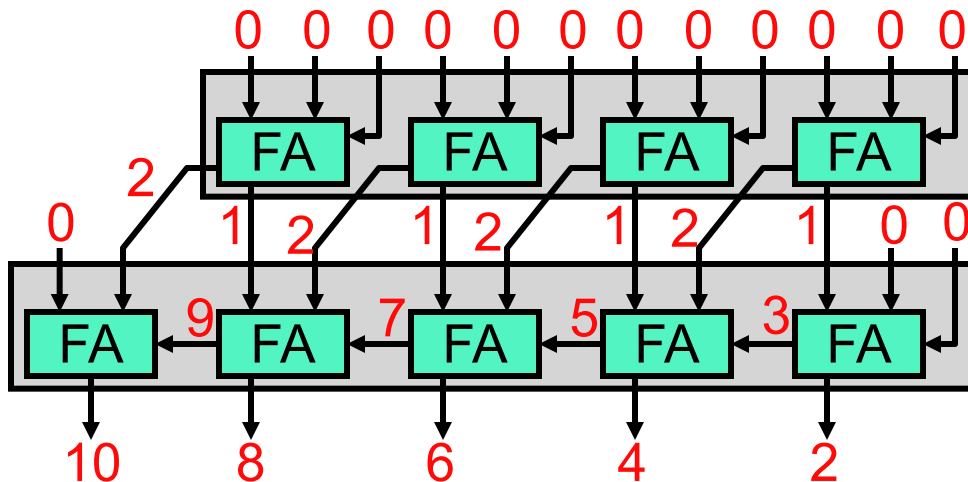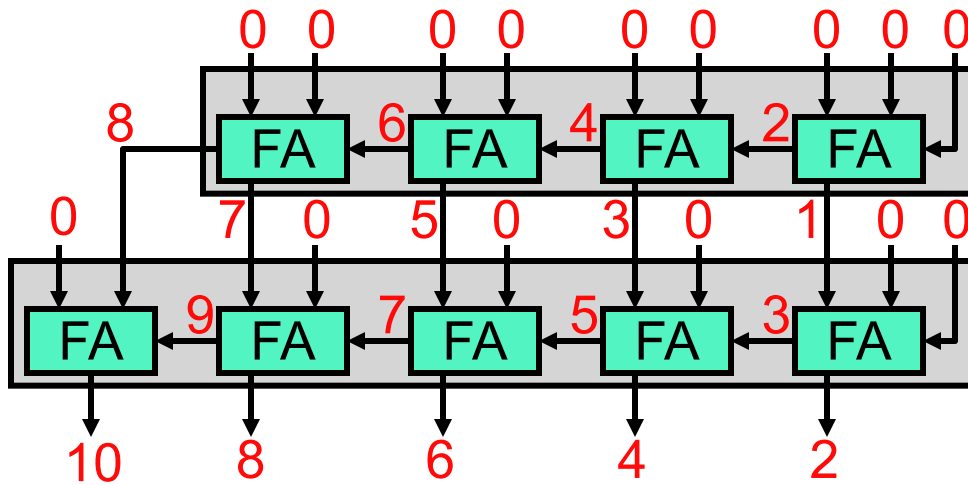


- CSA isn't faster :-(
  - why not?



# Let's use CLA instead of RC

 

 
- 4-bit CLA
  - all outputs available at the same time, after 4 gate delays
  - see slide [45. Two-Level CLA for 4-bit Adder](#)




- Now CSA helps
  - even large gains with more/larger numbers to add
 
# CSA Tree Multiplier


- Use 3-to-2 CSA adders
  - Build a tree structure
  - called a "Wallace Tree"
- 16-bit
  - Start: 16 bits
  - 1<sup>st</sup>:  $5 \times (3 \rightarrow 2) + 1 = 11$
  - 2<sup>nd</sup>:  $3 \times (3 \rightarrow 2) + 2 = 8$
  - 3<sup>rd</sup>:  $2 \times (3 \rightarrow 2) + 2 = 6$
  - 4<sup>th</sup>:  $2 \times (3 \rightarrow 2) + 0 = 4$
  - 5<sup>th</sup>:  $1 \times (3 \rightarrow 2) + 1 = 3$
  - 6<sup>th</sup>:  $1 \times (3 \rightarrow 2) + 0 = 2$
  - 7<sup>th</sup>: CLA
  - delay:  $2 + (6 \times 2) + 8 = 22$



# Consecutive Addition: Carry Save Adder

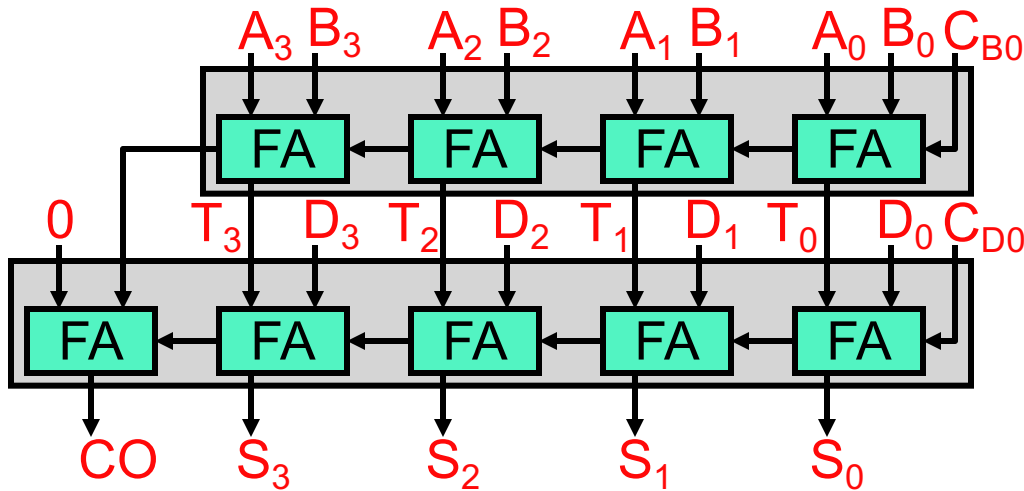

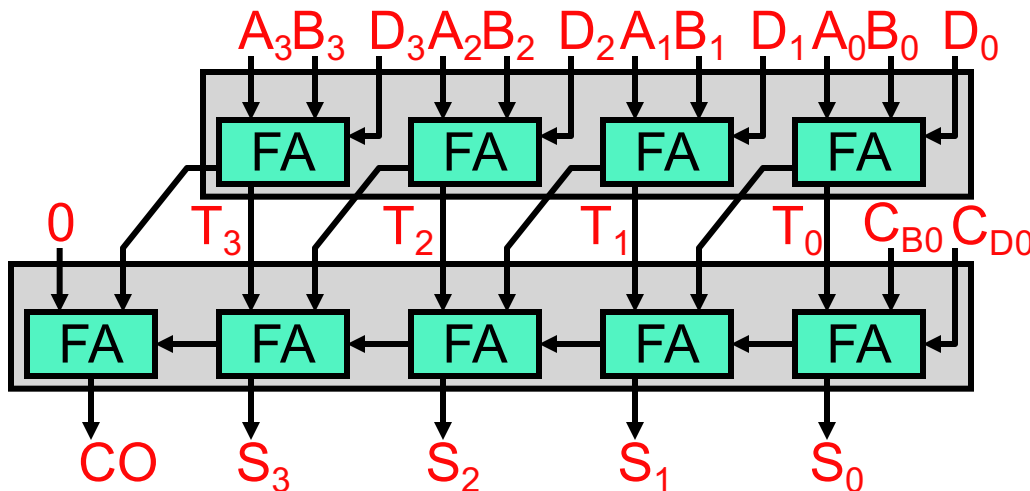- 2 N-bit RC adders  
+ 2 + d(add) gate delays
- M N-bit RC adders delay
  - Naïve:  $O(M*N)$
  - Actual:  $O(M+N)$



- M N-bit Carry Select?
  - Delay calculation tricky
- Carry Save Adder (CSA)
  - 3-to-2 CSA tree + adder
  - Delay:  $O(\log M + \log N)$

# Floating Point

# Floating Point (FP) Numbers

---

- **Floating point numbers:** numbers in scientific notation
  - Two uses
- Use I: real numbers (numbers with non-zero fractions)
  - 3.1415926...
  - 2.1878...
  - $6.62 * 10^{-34}$
- Use II: really big numbers
  - $3.0 * 10^8$
  - $6.02 * 10^{23}$
- Aside: best not used for currency values

# Scientific Notation

---

- **Scientific notation:**
  - Number  $[S,F,E] = S * F * 2^E$
  - S: **sign**
  - F: **significand** (fraction)
  - E: **exponent**
  - **“Floating point”**: binary (decimal) point has different magnitude
- + “Sliding window” of precision using notion of **significant digits**
  - Small numbers very precise, many places after decimal point
  - Big numbers are much less so, not all integers representable
  - But for those instances you don’t really care anyway
- Caveat: all representations are just approximations
  - Sometimes wierdos like 0.9999999 or 1.0000001 come up
- + But good enough for most purposes

# IEEE 754 Standard Precision/Range

---

- **Single precision:** `float` in C
  - 32-bit: 1-bit sign + 8-bit exponent + 23-bit significand
  - Range:  $2.0 * 10^{-38} < N < 2.0 * 10^{38}$
  - Precision:  $\sim 7$  significant (decimal) digits
  - Used when exact precision is less important (e.g., 3D games)
- **Double precision:** `double` in C
  - 64-bit: 1-bit sign + 11-bit exponent + 52-bit significand
  - Range:  $2.0 * 10^{-308} < N < 2.0 * 10^{308}$
  - Precision:  $\sim 15$  significant (decimal) digits
  - Used for scientific computations
- Numbers  $> 10^{308}$  don't come up in many calculations
  - $10^{80} \sim$  number of atoms in universe

# Floating Point is Inexact

---

- Accuracy problems sometimes get bad
  - FP arithmetic not associative:  $(A+B)+C$  not same as  $A+(B+C)$
  - Addition of big and small numbers (summing many small numbers)
  - Subtraction of two big numbers
- Example, what's  $(1*10^{30} + 1*10^0) - 1*10^{30}$ ?
  - Intuitively:  $1*10^0 = 1$
  - But:  $(1*10^{30} + 1*10^0) - 1*10^{30} = (1*10^{30} - 1*10^{30}) = 0$
- Reciprocal math: "x/y" versus "x\*(1/y)"
  - Reciprocal & multiply is faster than divide, but less precise
- Compilers are generally conservative by default
  - GCC flag: `-ffast-math` (allows assoc. opts, reciprocal math)
- **Numerical analysis**: field formed around this problem
  - Re-formulating algorithms in a way that bounds numerical error
- In your code: never test for equality between FP numbers
  - Use something like: `if (abs(a-b) < 0.00001) then ...`



# Pentium FDIV Bug

---

- Pentium shipped in August 1994
- Intel actually knew about the bug in July
  - But calculated that delaying the project a month would cost ~\$1M
  - And that in reality only a dozen or so people would encounter it
  - They were right... but one of them took the story to EE times
- By November 1994, firestorm was full on
  - IBM said that typical Excel user would encounter bug every month
    - Assumed 5K divisions per second around the clock
  - People believed the story
  - IBM stopped shipping Pentium PCs
- By December 1994, Intel promises full recall
  - Total cost: ~\$550M

# Arithmetic Latencies

---


- Latency in cycles of common arithmetic operations
- Source: *Agner Fog*,  
<https://www.agner.org/optimize/#manuals>
  - AMD Ryzen core

|              | Int 32 | Int 64 | Fp 32 | Fp 64 |
|--------------|--------|--------|-------|-------|
| Add/Subtract | 1      | 1      | 5     | 5     |
| Multiply     | 3      | 3      | 5     | 5     |
| Divide       | 14-30  | 14-46  | 8-15  | 8-15  |

- Divide is **variable latency** based on the size of the dividend
  - Detect number of leading zeros, then divide
- Why is FP divide faster than integer divide?

# Summary

---

 

- Integer addition
  - Most timing-critical operation in datapath
  - Hardware  $\neq$  software
    - Exploit sub-addition parallelism
- Fast addition
  - Carry-select: parallelism in sum
- Multiplication
  - Chains and trees of additions
- Division
- Floating point
- Next: single-cycle datapath